

Experiment 1
Biasing of Common-Emitter Amplifiers
Laboratory Report for ENGE 312
Applications of Electronic Devices
George Fox University
Newberg, OR
Jan 29, 2026

Daniel Blue, Ethan Searls, Levi Interian-Uc

I. PROJECT DESCRIPTION

The gain and bias stability of a common-emitter amplifier circuit was investigated in this laboratory experience. The gain of the amplifier was measured and compared between β values. Max Voltage Swing ($V_{o,p-p}$) was also measured and compared between β values.

II. THEORETICAL BACKGROUND

Consider the circuit shown in Fig. 1. It is a bjt amplifier in the common-emitter configuration.

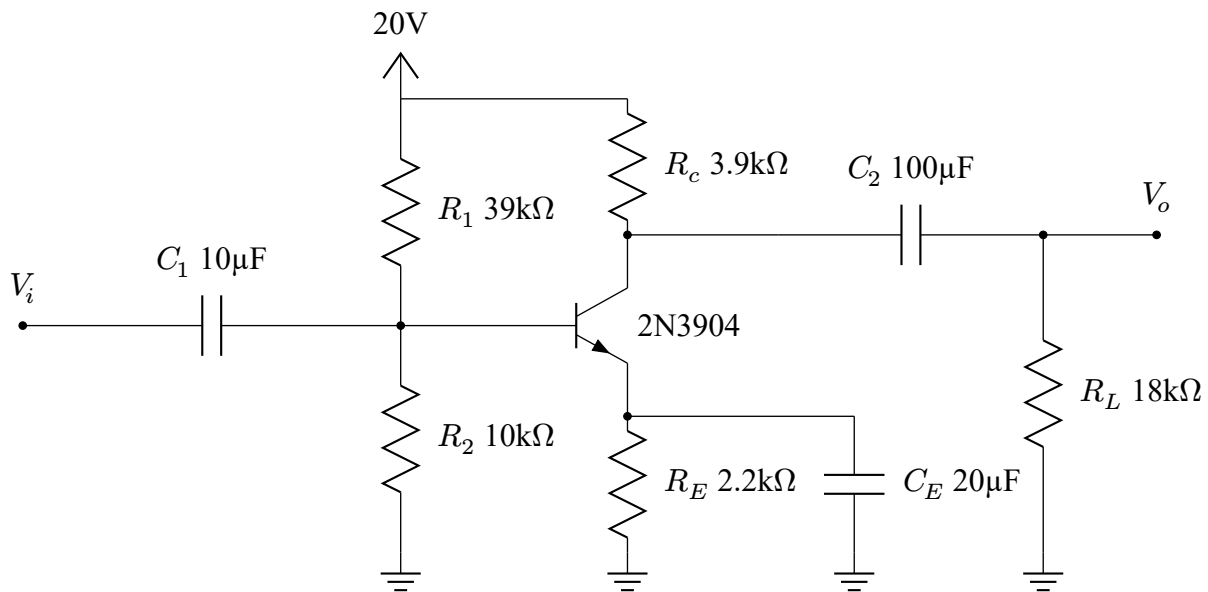


Fig. 1. BJT Amplifier in the Common Base Configuration

III. METHODS AND MATERIALS

A. Equipment

Your equipment table...

B. Experimental Procedure

Your procedure...

IV. RESULTS

A. Sample Calculations

(if needed)

V. DISCUSSION

Your discussion...

VI. CONCLUSIONS

Your conclusions...