

Experiment 3
Active Loading

Laboratory Report for ENGE 312
Applications of Electronic Devices
George Fox University
Newberg, OR
Feb 05, 2026

Daniel Blue, Ethan Searls, Levi Interian-Uc

I. RESULTS: SAMPLE CALCULATIONS

A. 1. Resistor Biased “CE” Amplifier

Given:

- $V_{CC} = 15 \text{ V}$
- $R_1 = 47 \text{ k } \Omega$, $R_2 = 33 \text{ k } \Omega$
- $R_C = 2.2 \text{ k } \Omega$, $R_E = 1.8 \text{ k } \Omega$, $R_L = 2.2 \text{ k } \Omega$
- Transistor Q_1 (2N3904): Assume $\beta \approx 130$, $V_{BE} \approx 0.7 \text{ V}$

Thevenin Equivalent Base Circuit:

$$R_B = R_1 \parallel R_2 = \frac{47 \text{ k} \cdot 33 \text{ k}}{47 \text{ k} + 33 \text{ k}} \approx 19.39 \text{ k } \Omega \quad (1)$$

$$V_{BB} = V_{CC} \cdot \frac{R_2}{R_1 + R_2} = 15 \text{ V} \cdot \frac{33}{80} = 6.19 \text{ V} \quad (2)$$

Q-Point Analysis:

$$\begin{aligned} I_{CQ} &= \frac{V_{BB} - V_{BE}}{R_E + \frac{R_B}{\beta}} \\ &= \frac{6.19 \text{ V} - 0.7 \text{ V}}{1.8 \text{ k } \Omega + \frac{19.39 \text{ k } \Omega}{130}} \\ &= \frac{5.49 \text{ V}}{1.8 \text{ k } \Omega + 0.15 \text{ k } \Omega} \\ &= 2.81 \text{ mA} \end{aligned} \quad (3)$$

$$\begin{aligned} V_{CE} &= V_{CC} - I_{CQ}(R_C + R_E) \\ &= 15 \text{ V} - 2.81 \text{ mA}(2.2 \text{ k } \Omega + 1.8 \text{ k } \Omega) \\ &= 15 \text{ V} - 11.24 \text{ V} \\ &= 3.76 \text{ V} \end{aligned} \quad (4)$$

AC Gain (A_V):

$$V_T \approx 26 \text{ mV} \quad (5)$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{2.81 \text{ mA}}{26 \text{ mV}} \approx 0.108 \text{ S} \quad (6)$$

$$R_{ac} = R_C \parallel R_L = \frac{2.2 \text{ k} \cdot 2.2 \text{ k}}{2.2 \text{ k} + 2.2 \text{ k}} = 1.1 \text{ k } \Omega \quad (7)$$

$$\begin{aligned}
 A_V &= -g_m(R_{ac}) \\
 &= -(0.108 \text{ S})(1100\Omega) \\
 &= -118.8
 \end{aligned} \tag{8}$$

Output Swing:

$$V_{o, \max} = V_{CE} - V_{CE, \text{sat}} \approx 3.76 \text{ V} - 0.2 \text{ V} = 3.56 \text{ V} \tag{9}$$

$$V_{o, \min} = I_{CQ}(R_C \parallel R_L) = (2.81 \text{ mA})(1.1 \text{ k } \Omega) = 3.09 \text{ V} \tag{10}$$

$$\begin{aligned}
 V_{o, \text{p-p}} &= 2 \cdot \min(V_{o, \max}, V_{o, \min}) \\
 &= 2 \cdot 3.09 \text{ V} = 6.18 \text{ V}
 \end{aligned} \tag{11}$$

B. 2. Current Mirror (Active Load Setup)

Given:

- Target $I_o \approx I_{CQ} \approx 2.81 \text{ mA}$ (matching the “CE” stage)
- $V_{CC} = 15 \text{ V}$
- Q_2, Q_3 (2N3906): Assume $\beta \approx 150$, $V_{BE} \approx 0.7 \text{ V}$

Reference Current Setting: To match I_o to I_{CQ} , we calculate the required R_{ref} :

$$\begin{aligned}
 R_{\text{ref}} &= \frac{V_{CC} - V_{BE}}{I_{\text{ref}}} \\
 &\approx \frac{15 \text{ V} - 0.7 \text{ V}}{2.81 \text{ mA}} \\
 &= 14.3 \frac{\text{V}}{2.81} \text{ mA} \\
 &= 5.09 \text{ k } \Omega
 \end{aligned} \tag{12}$$

(Note: In lab, use a potentiometer or series resistors to approximate 5.1 k Ω)

Output Current:

$$I_o = \frac{I_{\text{ref}}}{1 + \frac{2}{\beta}} = \frac{2.81 \text{ mA}}{1 + \frac{2}{150}} \approx 2.77 \text{ mA} \tag{13}$$

C. 3. “CE” Amplifier with Active Load (Current Source Biasing)

Given:

- Load $R_L = 2.2 \text{ k } \Omega$
- Bias $I_C \approx 2.8 \text{ mA}$
- Assume Early Voltage resistance $r_o = 30 \text{ k } \Omega$ for all transistors[cite: 49].

Voltage Gain with Active Load: The “ac”tive load repl“ac”es R_C with the output resistance of the current mirror (r_o of PNP).

$$\begin{aligned} R_{\text{eff}} &= r_{o, \text{NPN}} \parallel r_{o, \text{PNP}} \parallel R_L \\ &= 30 \text{ k } \Omega \parallel 30 \text{ k } \Omega \parallel 2.2 \text{ k } \Omega \\ &= 15 \text{ k } \Omega \parallel 2.2 \text{ k } \Omega \\ &= \frac{15 \text{ k} \cdot 2.2 \text{ k}}{15 \text{ k} + 2.2 \text{ k}} \approx 1.92 \text{ k } \Omega \end{aligned} \tag{14}$$

$$\begin{aligned} A_V &= -g_m(R_{\text{eff}}) \\ &= -(0.108 \text{ S})(1920\Omega) \\ &= -207.4 \end{aligned} \tag{15}$$

(Note: The gain increases significantly compared to the resistor biased version (119 vs 207) due to the higher “eff”ective AC impedance at the collector, even though R_L dominates in this loaded case.)

II. DISCUSSION

III. APPENDIX